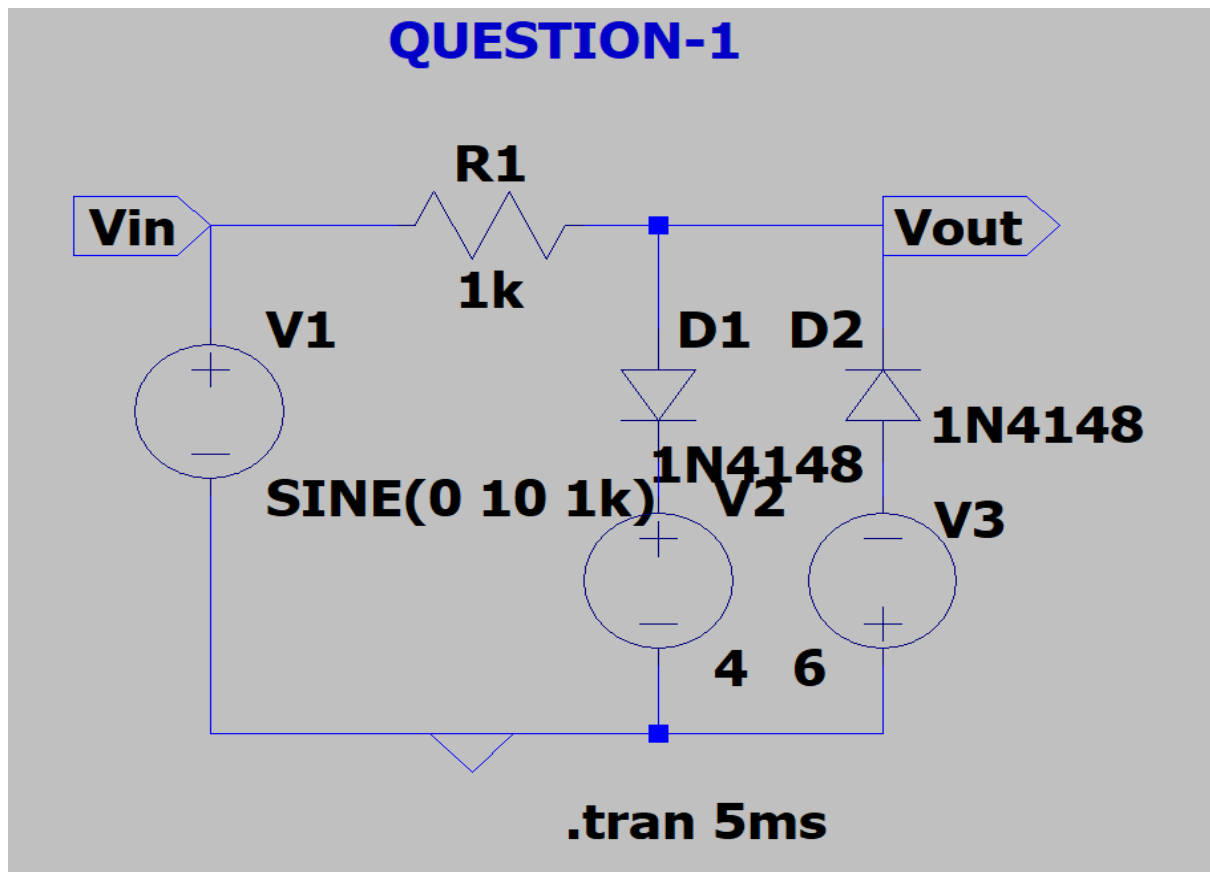


# EEE VT


By: Amogh Garg(2020UCO1688)

## QUESTION 1:

Circuit:




Output:

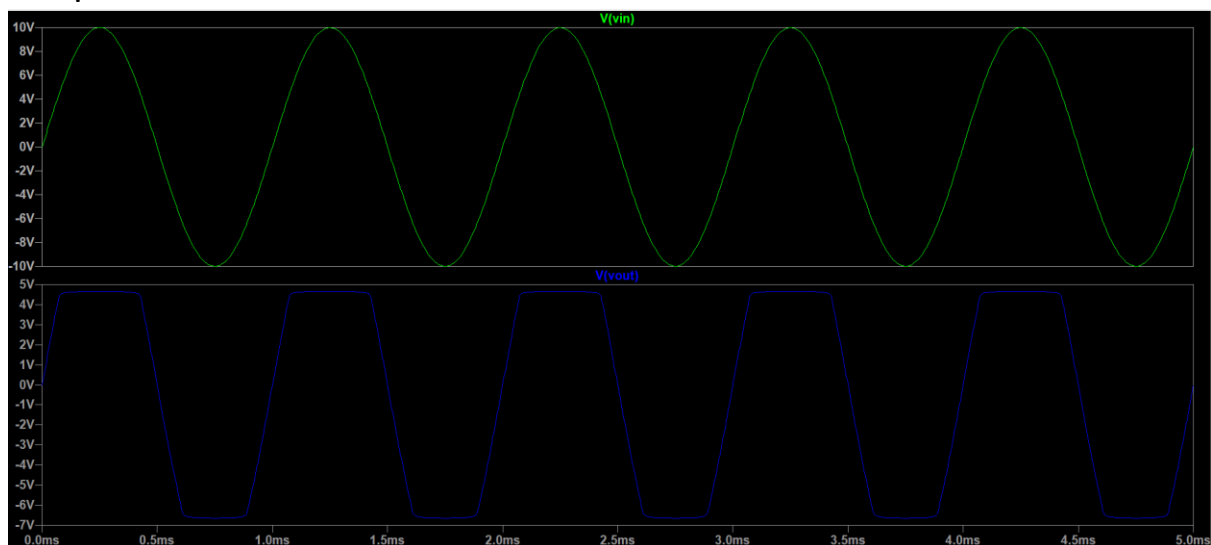


## QUESTION-2:

Circuit:

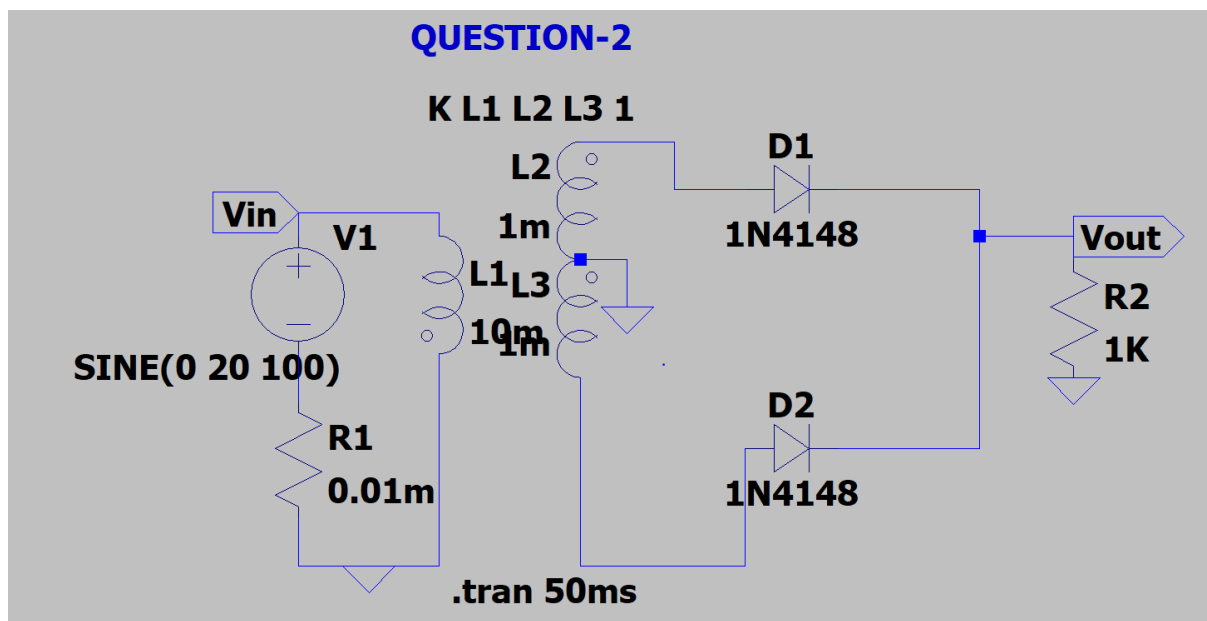

Output:

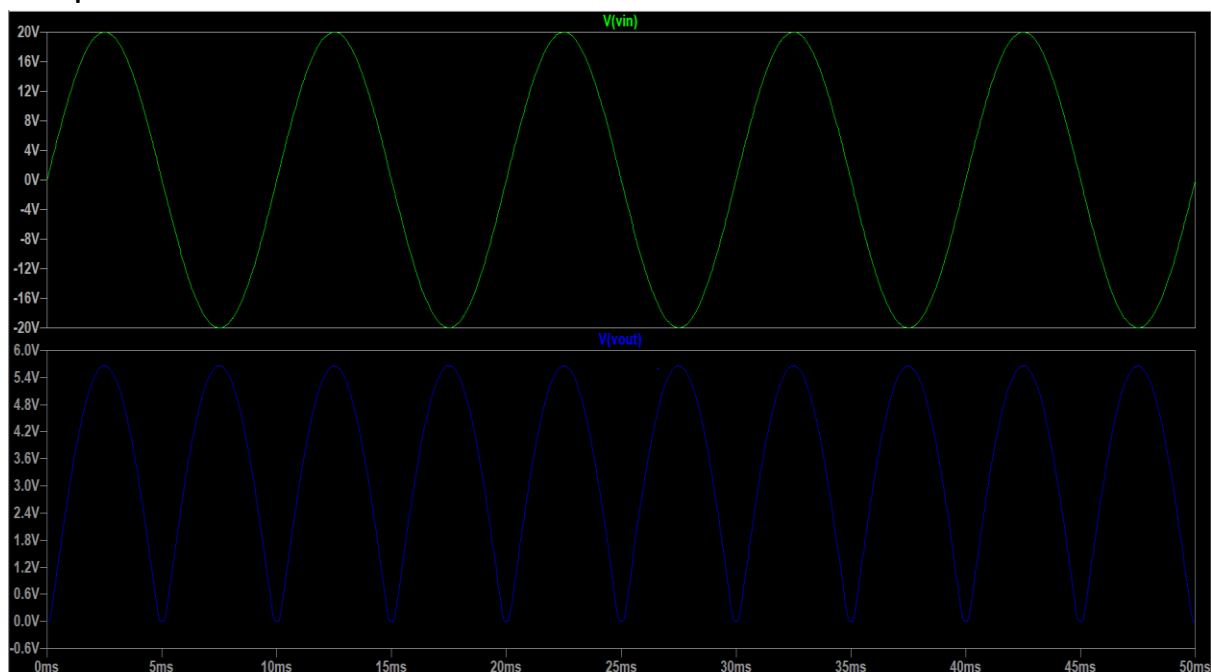

By: Amogh Garg

2020UCO1688

COE (SECTION-3)