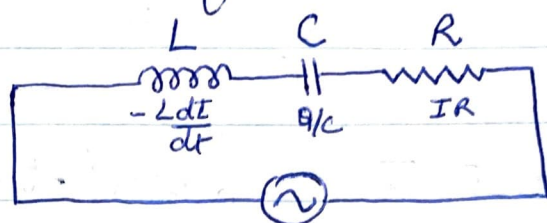


Application of Resonance in LCR ckt



$$E = E_0 \sin pt$$

Applied alternating voltage.

Let I be the current in the circuit at any instant and Q be the charge on the plates of the capacitor then potential drop across various components will satisfy the eqn:

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = E = E_0 \sin pt \quad \text{--- (1)}$$

Since $I = \frac{dQ}{dt}$ we get:

$$\frac{d^2Q}{dt^2} + \left(\frac{R}{L}\right) \frac{dQ}{dt} + \frac{Q}{LC} = \left(\frac{E_0}{L}\right) \sin pt$$

This is similar to forced oscillator eqn. where x replaced by Q , etc.

Steady state soln. can be obtained by same substitutions:

$$Q = \frac{E_0/L}{\sqrt{\left(\frac{1}{LC} - p^2\right)^2 + \left(\frac{PR}{L}\right)^2}} \sin(pt - \phi)$$

$$\phi = \tan^{-1} \frac{\omega R / L}{\frac{1}{LC} - \omega^2}$$

Let current $I = I_0 \sin(\omega t - \phi)$

$$\frac{dI}{dt} = I_0 \omega \cos(\omega t - \phi)$$

and $Q = \int I dt = -\frac{I_0}{\omega} \cos(\omega t - \phi)$

Put these values in eqn (1)

$$L I_0 \omega \cos(\omega t - \phi) + R I_0 \sin(\omega t - \phi)$$

$$= \frac{I_0}{\omega C} \cos(\omega t - \phi) = E_0 \sin \omega t$$

$$I_0 \left[R \sin(\omega t - \phi) + \left(L\omega - \frac{1}{C\omega} \right) \cos(\omega t - \phi) \right] = E_0 \sin \omega t$$

Put $R = a \cos \phi$ $L\omega - \frac{1}{C\omega} = a \sin \phi$ — (2)

$$I_0 a [\cos \phi \sin(\omega t - \phi) + \sin \phi \cos(\omega t - \phi)] = I_0 a \sin[(\omega t - \phi) + \phi] = E_0 \sin \omega t$$

Just like forced oscillation, square & add eqns (2) :-

$$a = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2} \quad \tan \phi = \frac{\left(L\omega - \frac{1}{C\omega} \right)}{R}$$

Putting these in above eqn.

$$I_0 \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} \sin \omega t = E_0 \sin \omega t$$

$$I_0 \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} = E_0$$

$$I_0 = \frac{E_0}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$I = I_0 \sin(\omega t - \phi) = \downarrow \sin(\omega t - \phi)$$

$\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$ is equivalent to

the effective resistance of LCR ckt.
It is k/a the impedance, Z .

It has two terms :-

- 1) Freq. independent ohmic R .
- 2) " dependant reactance (X)

$$X = L\omega - \frac{1}{C\omega}$$

This also has two parts, inductive reactance (X_L) & capacitive reactance (X_C)

$$X = X_L + X_C$$

$$Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + (X_L - X_C)^2}$$

Peak value of current:

$$I_0 = \frac{E_0}{Z}$$

$$I = \frac{E_0}{Z} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

Case I :

$X_L = X_C$, then $Z = R$ and current is max. Cond. of Resonance.

$$I_0 = \frac{E_0}{R}$$

$$I_0 \rightarrow \infty \text{ as } R \rightarrow 0$$

and no phase diff b/w current and emf.

$$X_L = X_C \Rightarrow L\omega = \frac{1}{C\omega}$$

$$\omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\text{Resonant freq} = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

Case - II -

$X_L > X_C$ then net reactance is inductive, and $\tan \phi$ is positive. Current lags behind emf.

Case III

$X_L < X_C$; then net reactance is capacitive, $\tan \phi$ is negative current leads the emf.

